



BARISHAL ENGINEERING COLLEGE

Department of Electrical & Electronic Engineering

LAB REPORT

Course Title : Electrical Circuit II sessional.

Course Code : EEE-1202

Experiment No. : 01

Name of Experiment : To study the frequency response of series RLC circuit & determine the resonance frequency.

Date of Experiment : 09-12-2021

Submitted By

Name : Muhammad Jobayed Ibna
Barshar

Class Roll : 192097

Exam Roll :

Reg. No. : 3145

Session : 2019-20

Semester : 2nd

Submitted To

Rabeya Akter

Assistant Professor

Dept. of EEE

Barisal Engineering College.

Date of Submission : 6-01-2022

Signature

Name of Experiment: To study the frequency response of series RLC circuit & determine the resonance frequency.

Aim: To observe the frequency response of a series RLC circuit & determine the resonance frequency of a series RLC circuit

Apparatus: (i) Audio frequency Generator.
(ii) CRO.
(iii) Multimeter.
(iv) Connecting wires/leads.
(v) AC power supply (Single phase)

Theory: In the series resonance circuit, the net reactance, $X = X_L - X_C$

So, The impedance of the circuit, $Z = \sqrt{R^2 + (X_L - X_C)^2}$

At the resonance frequency the capacitive reactance becomes equal to the inductive reactance.

$$X_L = X_C$$

$$\Rightarrow \omega_0 L = \frac{1}{\omega_0 C}$$

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Circuit diagram:

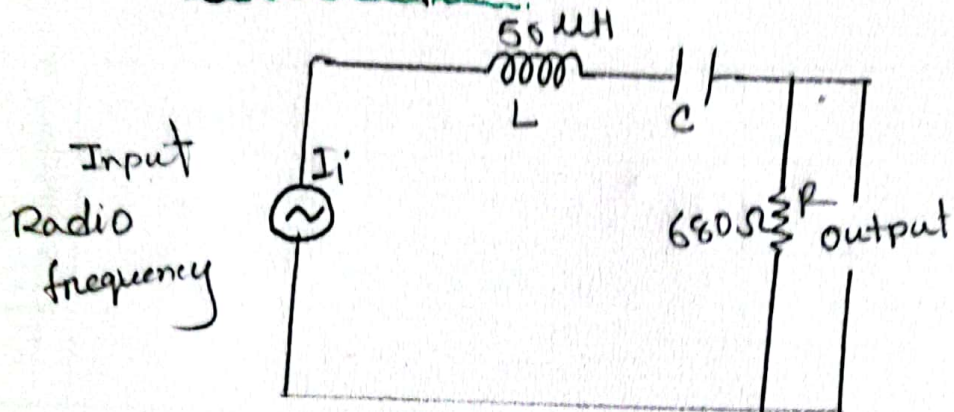


Figure:- Series RLC circuit

Procedure: (1) Make the connection as shown in figure.

(2) Frequency is given by the audio frequency generator.

(3) Change the frequency & note the reading carefully.

(4) At certain frequency voltage become max after which the voltage decrease. This is the resonance frequency.

(5) Plot a graph between plot & voltage.


(6) Now, change value of resistor & repeat the procedure 3-5 for several values of R.

Data table :-

SL NO	Value of R	Frequency (GHz)	voltage (volts)
1	1.2 k Ω	22.26	3.2
2		49.82	3.4
3		94.38	3.3
1	1.5 k Ω	32.35	2.7
2		39.68	2.8
3		90.26	2.7
1	2 k Ω	25.50	1.9
2		46.64	2.1
3		71.28	1.7

Graph :-

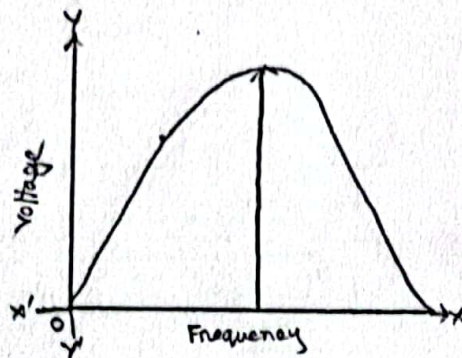According to ~~all~~ graph, the graph will like this.



Precaution :- (i) All connection should be tight &


correct.

(ii) Switch off the supply when not in used,

(iii) Reading should be taken carefully

Data table:

f R	Frequency (GHz)	voltage (volts)
	22.26	3.2
1.2	49.82	3.4

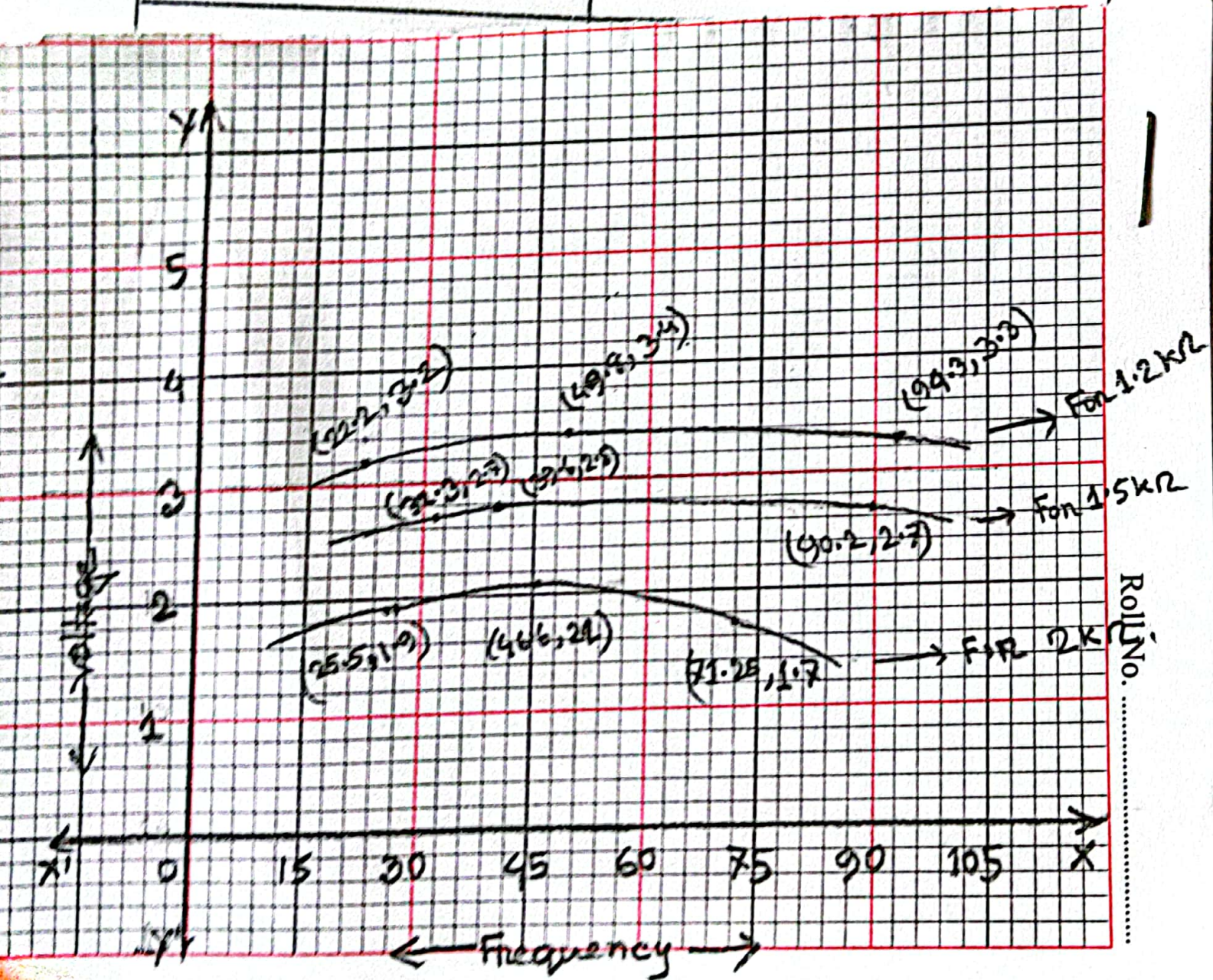

Roll No.



BARISHAL ENGINEERING COLLEGE

Department of Electrical & Electronic Engineering

LAB REPORT

Course Title : Electrical Circuits II sessional .

Course Code : EEE -1202

Experiment No. : 02

Name of Experiment : To study the frequency response of parallel RLC circuit & determine the resonance frequency

Date of Experiment : 23-12-2021

Submitted By

Name : Muhammad Jobayed Ibra
Bashar

Class Roll : 192097

Exam Roll :

Reg. No. : 3115

Session : 2019-20

Semester : 2nd

Submitted To

Rabeya Akter

Assistant Professor

Dept of EEE

Barishal Engineering College.

Date of Submission : 6-01-2022

Signature

Name of experiment: To study the frequency response of parallel RLC circuit & determine the resonance frequency.

Aim: To observe the frequency response of parallel RLC circuit and determine the resonance frequency of parallel RLC circuit.

Apparatus: (i) Audio frequency generator.
(ii) CRO.
(iii) Multimeter.
(iv) connecting wires.
(v) AC power supply. (Single phase).

Theory: For the parallel RLC circuit,
 $I_c = I_L \sin \phi_L$

$$\text{Again, } I_c = \frac{V}{X_c} ; I_L = \frac{V}{Z}$$

$$\therefore \sin \phi_L = \frac{X_L}{Z}$$

$$\Rightarrow \frac{V}{Z} \times \frac{X_L}{Z} = \frac{V}{X_c}$$

$$\Rightarrow X_c \times X_L = Z^2$$


$$\text{Now, } X_L = \omega L, X_c = \frac{1}{\omega C}$$

$$\Rightarrow \frac{\omega L}{\omega C} = Z^2$$

$$\Rightarrow \frac{L}{C} = Z^2 = R^2 + X_L^2$$

$$\therefore f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$


Circuit Diagram:

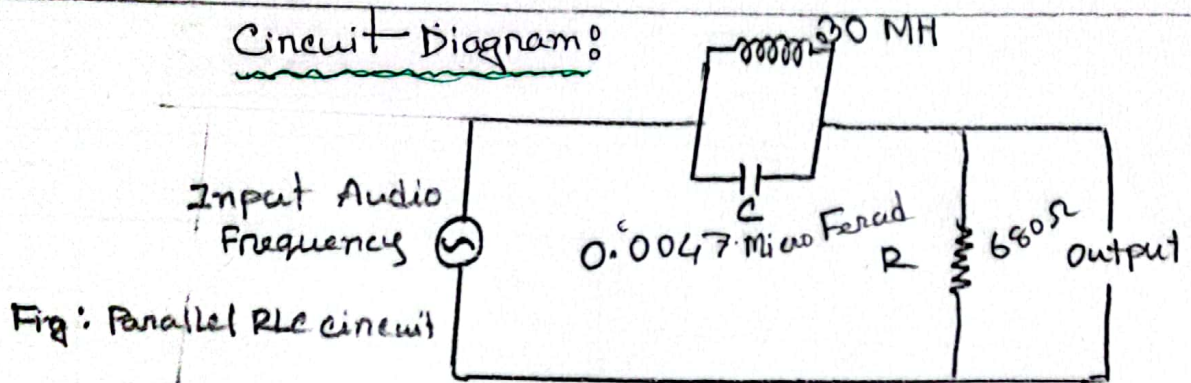

Procedure:

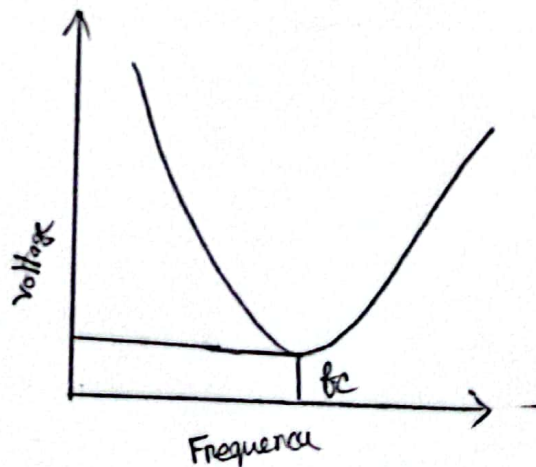- (i) Make the connections shown in figure.
- (ii) Frequency is given by the audio frequency generation.
- (iii) Change the frequency and note carefully.
- (iv) At the certain frequency voltage becomes minimum after which the voltage increases. This is frequency.
- (v) plot a graph between frequency and voltage.

Graph: According to these all graph, The graph will like this.



Data table:

Sl no	Resistance, R	Frequency (ω , Hz)	voltage (volts)
1	1.2 k Ω	32.46	2.9
2		46.33	2.2
3		88.12	2.5
1	1.5	26.13	2.6
2		49.32	2.4
3		79.15	3.1
1	2	34.75	3.8
2		61.26	3.1
3		94.62	3.6

Precaution:

- (i) All connectors should be tight and correct.
if not used.
- (ii) Switch off the supply when carefully.
- (iii) Reading should be taken

a table:

R	Frequency (ω Hz)	voltage (volts)
R	32.46	2.9
	46.33	2.2
	88.12	2.5
R	26.13	2.6
	49.32	2.4
		2.4

