

1

☐ Name of the experiment : To analyze the frequency response of a RLC Bandpass filter.

☐ Objective : After completing this experiment, we will know the effect of input frequency to the output of a B.P.F. We will also know how to draw a semi-log graph of frequency vs function.

☐ Theory : A Bandpass filter is a circuit that pass all the frequencies within a band of frequencies ($\omega_1 < \omega < \omega_2$). A B.P.F is formed when the output of a RLC series circuit is taken off the resistor shown in

Fig: (1)

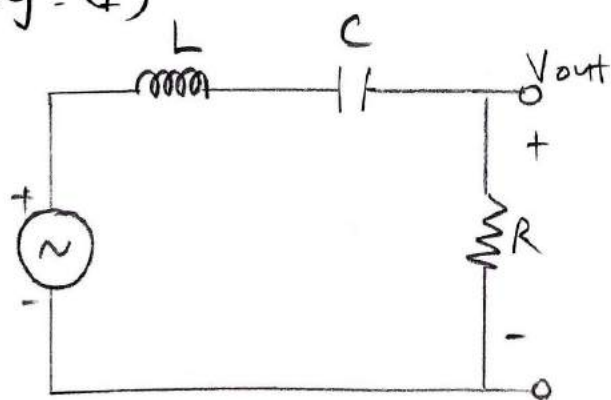


Fig: (1)

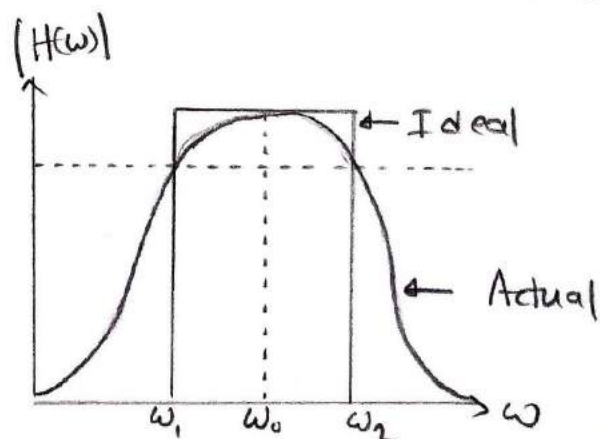


Fig: (2)

In fig(2), the frequency vs gain graph showing the ideal and actual frequency response of a Bandpass filter.

For a P.B.F, the center frequency,

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \text{--- (i)}$$

$$B = \frac{R}{L} \quad \text{--- (ii)}$$

$$\omega_1 = \omega_0 - \frac{B}{2}, \quad \omega_2 = \omega_0 + \frac{B}{2}$$

$$\Rightarrow f_1 = \frac{\omega_1}{2\pi} \quad \text{--- (iii)} \quad \Rightarrow f_2 = \frac{\omega_2}{2\pi} \quad \text{--- (iv)}$$

Taking 5V as input voltage, $L=330\mu\text{H}$, $C=30\mu\text{F}$
 $R=2.4\ \Omega$, the required circuit will be same as fig(3).

Apparatus:

1. Frequency generator
2. Oscilloscope
3. Resistor
4. Capacitor
5. Inductor
6. Breadboard
7. Connector

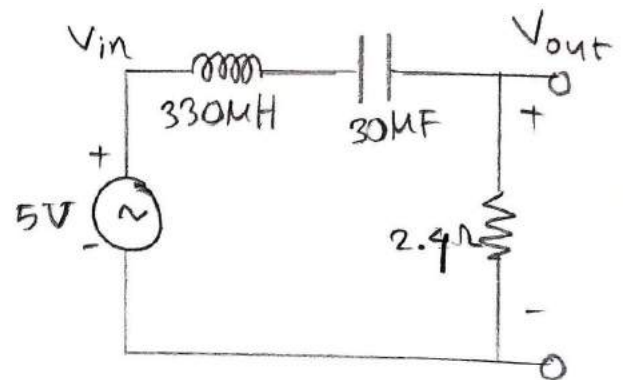



Fig:(3)

Procedure:

1. Make the circuit and connect the frequency generator to the output.
2. To measure the frequency response, connect CH-1 and CH-2 of oscilloscope to input and output respectively.
3. Go to the 'measure' function of oscilloscope and set the peak-to-peak voltages of CH-1 and CH-2 to display.
4. For a wide range of frequency, in both side of f_1 and f_2 , note the peak-to-peak voltages (V_{PP}) of CH-1 and CH-2 and make a data table of frequency, $V_{PP}(in)$, $V_{PP}(out)$, and gain.
5. From the experimental value, draw a semi-log graph of frequency vs gain.

Data table of Bandpass

	Frequency (Hz)	V _{in} (PK-PK)	V _{out} (PK-PK)	$H(\omega) = \frac{V_o}{V_i}$
1	200	5	0.175	0.035
2	300	4.87	0.438	0.09
3	500	4.69	1.032	0.22
4	700	4.48	1.83	0.41
5	1K	4.35	2.856	0.68
6	1.5K	4.2	4.2	1
7	2.1K	4.01	2.76	0.69
8	3K	3.97	1.58	0.4
9	4K	3.88	1	0.26
10	6K	3.68	0.97	0.13
11	9K	3.58	0.21	0.06
12	20K	3.5	0.035	0.01

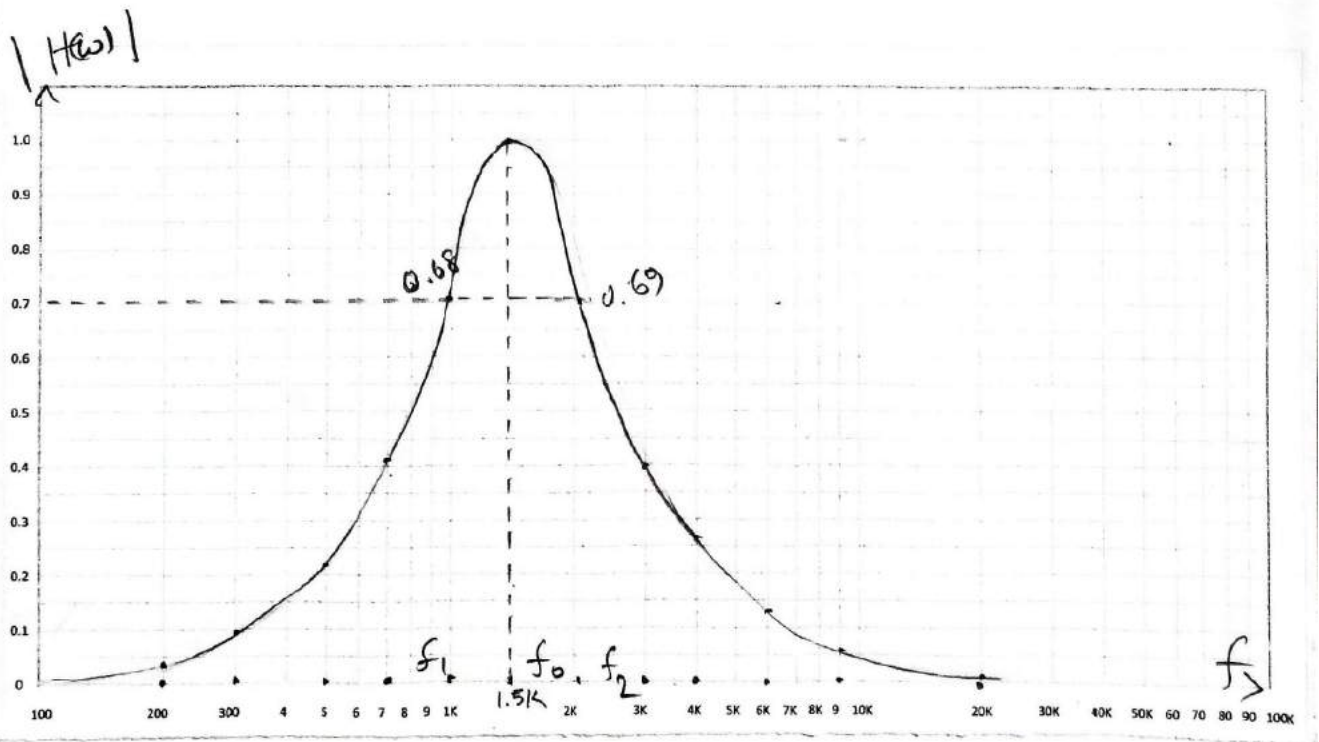

The semi-log graph of frequency vs gain.

☐ Calculation:

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{330 \times 30 \times 10^{-12}}} = 10 \text{ K rad/s}$$

$$\therefore f_0 = \frac{\omega_0}{2\pi} = 1.5 \times 10^3 \text{ Hz}$$

$$B = \frac{R}{L} = \frac{2.4}{330 \times 10^{-6}} = 7.27 \times 10^3$$

$$\begin{aligned} \omega_1 &= \omega_0 - \frac{B}{2} \\ &= 10 \times 10^3 - 3636 \\ &= 6363 \text{ rad/s} \end{aligned}$$

$$\begin{aligned} \omega_2 &= \omega_0 + \frac{B}{2} \\ &= 10 \times 10^3 + 3636 \\ &= 13636 \text{ rad/s} \end{aligned}$$

$$\begin{aligned} \therefore f_1 &= \frac{\omega_1}{2\pi} = 1012 \text{ Hz} \\ &\approx 1000 \text{ Hz} \end{aligned}$$

$$\begin{aligned} \therefore f_2 &= \frac{\omega_2}{2\pi} = 2170 \\ &\approx 2100 \text{ Hz} \end{aligned}$$

☐ Result: The circuit is a RLC Bandpass filter from 1000 Hz to 2100 Hz.

☐ Precaution:

1. Make sure the sine wave is selected
2. Set both the coaxial cables of oscilloscope either 1x or 10x mode.
3. Make sure, both ch-1 and ch-2 is on.