

1

Name of the experiment: To analyze the frequency response of a RLC Bandstop filter.

Objective: After completing this experiment, we will know the effect of input frequency to the output of a B.S.F. We will also know how to draw a semi-log graph of frequency vs transfer function.

Theory: A Bandstop filter is a circuit that eliminates all the frequencies within a band of frequencies ($\omega_1 < \omega < \omega_2$). A B.S.F is formed when the output of a RLC series circuit is taken over LC series combination shown in figure (1).

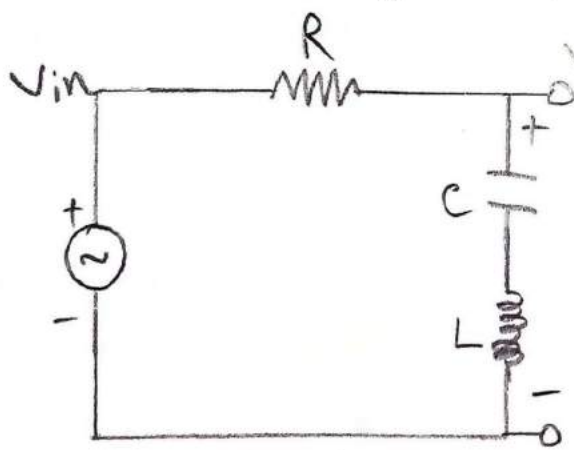


Fig: (1)

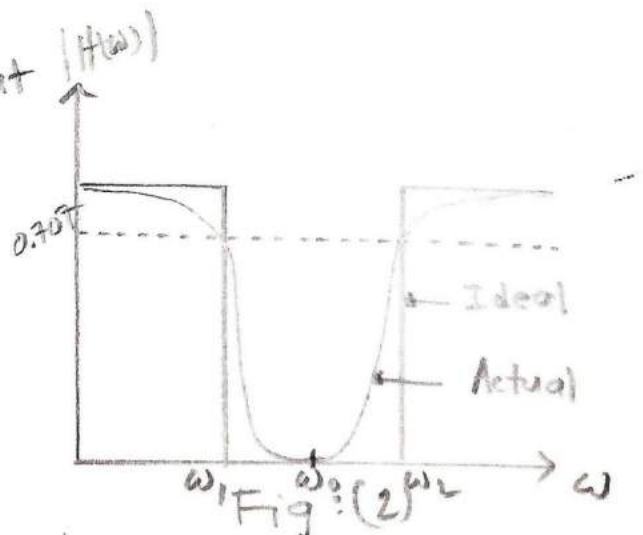


Fig: (2)

In fig.(2), the frequency vs gain graph showing the ideal and actual frequency response of a Bandstop filter.

For a B.S.F, the center frequency,

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \text{--- (i)}$$

$$B = \frac{R}{L} \quad \text{--- (ii)}$$

$$\omega_1 = \omega_0 - \frac{B}{2} \qquad \omega_2 = \omega_0 + \frac{B}{2}$$

$$\Rightarrow f_1 = \frac{\omega_1}{2\pi} \quad \text{--- (iii)} \qquad \Rightarrow f_2 = \frac{\omega_2}{2\pi} \quad \text{--- (iv)}$$

Taking $V(t) = 5V$, $L = 330\mu H$, $C = 30\mu F$, $R = 2.4\Omega$
the required circuit will be same as fig(3)

Apparatus:

1. Frequency generator
2. Oscilloscope
3. Resistor
4. Capacitor
5. Inductor
6. Breadboard
7. Connector




Fig: (3)

Procedure :

1. Make the circuit and connect the frequency generator to the input.
2. To measure the frequency response, connect CH-1 and CH-2 of oscilloscope to input and output respectively.
3. Go to the 'measure' function of oscilloscope and set the peak-to-peak voltages of CH-1 and CH-2 to display.
4. For a wide range of frequency, in both side of f_1 and f_2 , note the peak-to-peak voltages (V_{PP}) of CH-1, and CH-2 and make a data table of frequency, $V_{PP}(\text{in})$, $V_{PP}(\text{out})$ and gain (A_v).
5. From the experimental value, draw a semi-log graph of frequency vs gain.

Data table: Bandstop

	Frequency (Hz)	V _{in} (Pk-Pk)	V _{out} (Pk-Pk)	H(ω) = $\frac{V_o}{V_i}$
1	200	5		
2	300	4.87	4.55	0.97
3	500	4.69	4.58	0.94
4	700	4.48	4.08	0.87
5	1k	4.35	3.72	0.83
6	1.5k	4.2	2.95	0.68
7	2.1k	4.01	0.01	0.001
8	3k	3.97	2.76	0.69
9	4k	3.88	3.33	0.84
10	6k	3.68	3.53	0.91
11	9k	3.58	3.53	0.96
12	20k	3.5	3.5	0.98
			3.4	0.99

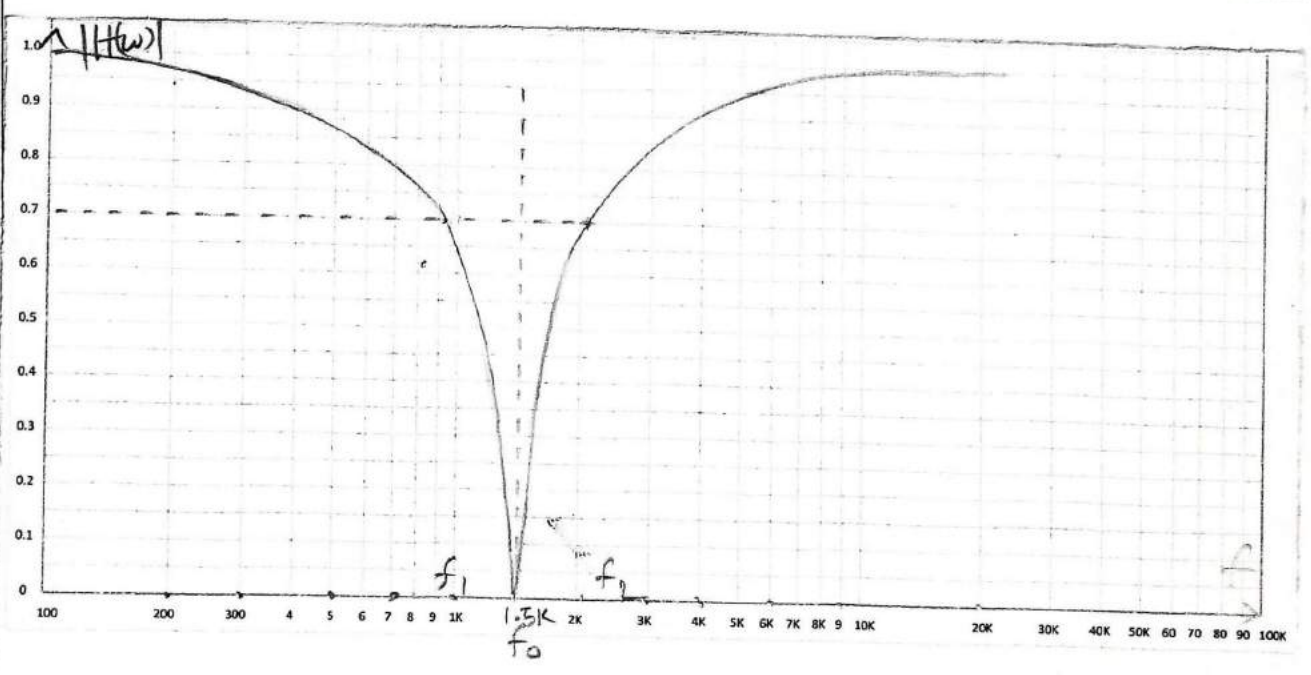

Calculation:

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{330 \times 30 \times 10^{-12}}} = 10000 \text{ rad/s}$$

$$\therefore f_0 = \frac{\omega_0}{2\pi} = 1.5 \times 10^3 \text{ Hz}$$

$$B = R/L = \frac{2.4}{330 \times 10^{-6}} = 7.27 \times 10^3$$

$$\therefore \omega_1 = \omega_0 - \frac{B}{2} = 10 \times 10^3 - 3636 \quad \left| \quad \omega_2 = \omega_0 + \frac{B}{2} = 10 \times 10^3 + 3636$$

$$= 6363 \text{ rad/s} \quad \quad \quad = 13636 \text{ rad/s}$$

$$\therefore f_1 = \frac{\omega_1}{2\pi} = 1012 \text{ Hz}$$

$$\approx 1000 \text{ Hz}$$

$$\therefore f_2 = \frac{\omega_2}{2\pi} = 2170$$

$$\approx 2100 \text{ Hz}$$

Result: The circuit is a RLC Bandstop Filter from 1000 Hz to 2100 Hz.

Precautions:

1. Make sure the sine wave is selected
2. Set both the coaxial cables of oscilloscope either 1x or 10x mode.
3. Make sure both channel 1 and channel 2 are on.